

## **Lesson 2.2 Summative Assessment Questions**

- 1. Which of these is classified as an output?
  - A. Switch
  - B. LED
  - C. Button
  - D. All of these are outputs
- 2. Which of these is an input?
  - A. Switch
  - B. Mouse
  - C. Button
  - D. All of these are inputs
- 3. What is the relationship between switches and buttons?
  - A. A switch completes a circuit but a button does not.
  - B. A button completes a circuit but a switch does not.
  - C. A button is a type of switch that can be pressed to complete a circuit.
  - D. A button can be pressed in a game but switches can't.
- 4. Which of these best describes what occurs with the electrical current flow when switches are turned on and off?
  - A. Current flows to the right when the switch is On and flows to the left when the switch is Off.
  - B. Current can be controlled to behave like binary and either be 1 = ON or 0 = OFF
  - C. Current flow cannot be controlled by turning a switch on or off.
  - D. Current runs through a circuit even when a switch it turned off.
- 5. Which of these statements is FALSE about the control of electricity for buttons and switches?
  - A. The button in our circuit needs to be held down to allow electricity to flow.
  - B. Switches hold a binary number (1 or 0) depending on the position of the switch (On or Off).
  - C. Buttons and switches cannot control the flow of electricity.
  - D. Buttons and switches control the flow of electricity when turned on and off.
- 6. Why do we need two wires per component connected on the breadboard?
  - A. To complete the circuit, electricity flows from the GPIO to the component on one wire, and from the component back to the GPIO on the other wire.
  - B. Because one wire would be lonely without the other.
  - C. In case one breaks we have a spare.
  - D. To complete the circuit, electricity flows from the GPIO through both wires to the component.
- 7. Which of these *best* describes how the game knows a switch or button is pressed?
  - A. The game doesn't know, it is programmed to randomly do stuff every second
  - B. The game is programmed to detect the state of the electricity going into the pin connected to the switch or button
  - C. The game reads minds and knows what we intended to do
  - D. The game is programmed to turn the output devices of switch and button on and off