



Phase 2 Visual Organizer (Overview)

StoryMode Level (Planet)	What circuit (or circuits) did you build? Draw it.	Describe how current flows through the circuit.	What does each component in the circuit do?
Mars			
Cheeseteroid			
Treasure Hunt			
Chain Reaction			
Power Plant			
Breadboard Bluffs			
Rainbow Bridge			
Funky Fungi			
Cheeseteroid Return			